

Abstract

The goal of this lab was to create a circuit in VHDL that uses combinational and sequential logic circuits. This was done by making a VHDL program that would output 4 signals that are unique from each other (figure 1). The program would take a 50 MHz clock, derive it to 50 kHz, then using that derived clock signal to output a sync signal, and 3 data signals on the FPGA output pins along with the clock signals. The output signals were then read on using the analog discovery to see if they match the desired output signals. In the end the lab was successful. We were able to successfully output the desired signals to the output pins on the FPGA pins with minor issues (figure 4).

The Process

To complete this lab, we first created a state diagram (figure 2) after realizing that the signals rely on a 3 bit counter. We drew the states and determined the output logic using k-maps. Although we could have just used conditional statements or case statements within the process to achieve the same function, I believe that this method used less lines to achieve the same goal. We used code made by Dr. Aamodt as a basis for the clock divider and the derived output logic to create the code. The signals were then sent out of Extout 0-4, Extout 7, Tek1 0-4, Tek1 7, and Tek5 (figure 3). The only errors we encountered were syntax errors that were easily corrected and an error in the output that was caused by the first and third bits of the 'Q' signal being swapped. We also found that the number of size flip flops used was 14 of 120800, the number of occupied slices was 8 of 15850, the number of bonded IOB pins was 19 of 300, the number of

BUFGs was 2 of 32, and the average fanout of non-clock nets was 2.54.

 


Figure 1: The desired output signals

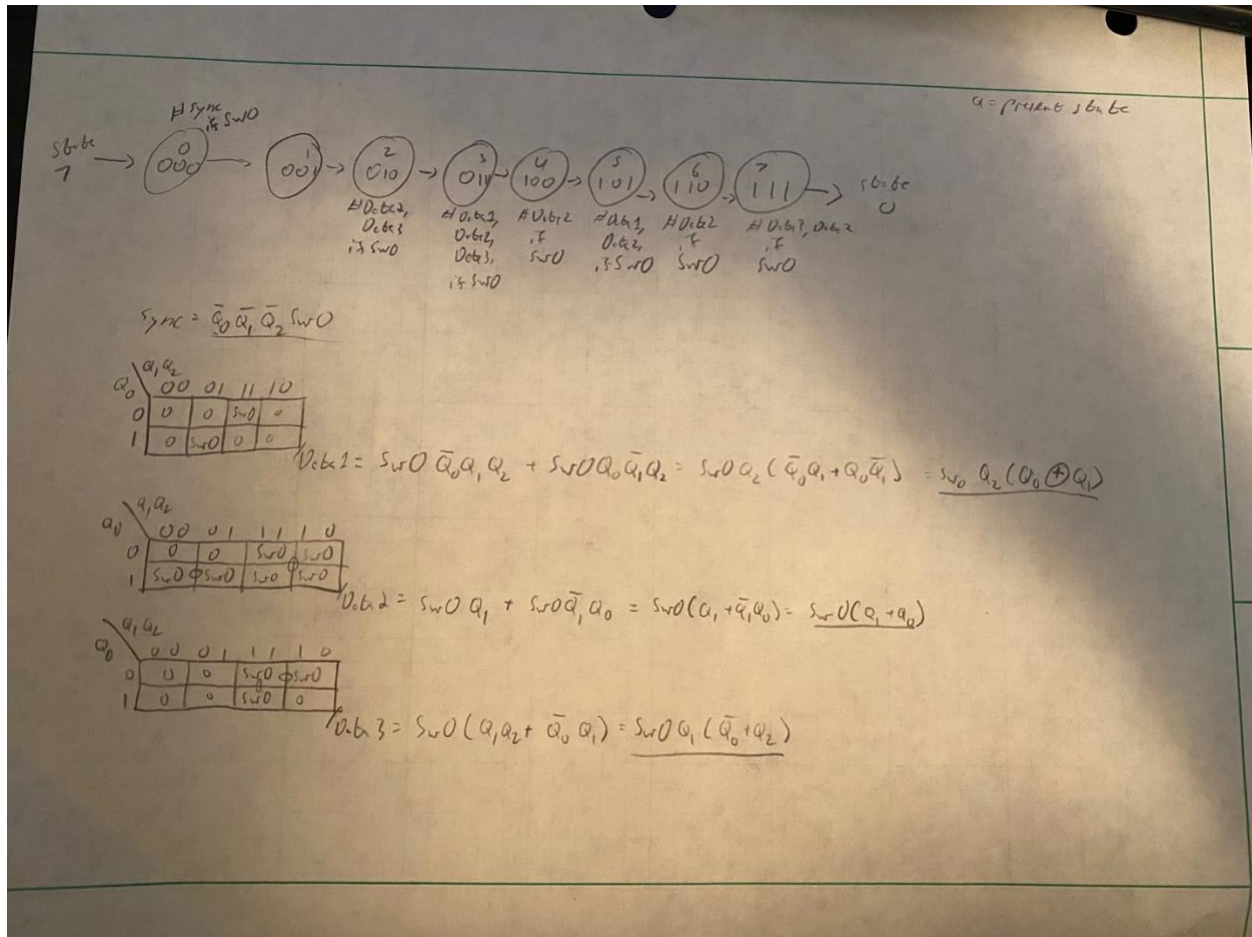


Figure 2: State diagram and output logic

Output Signal	Connections
Sync	Extout(0), TEK1(0)
Data1	Extout(1), TEK1(1)
Data2	Extout(2), TEK1(2)
Data3	Extout(3), TEK1(3)
Derived clock	Extout(4), TEK1(4)
Master clock (50Mhz)	Extout(7), TEK1(7), TEK5

Figure 3: The signals and their connections

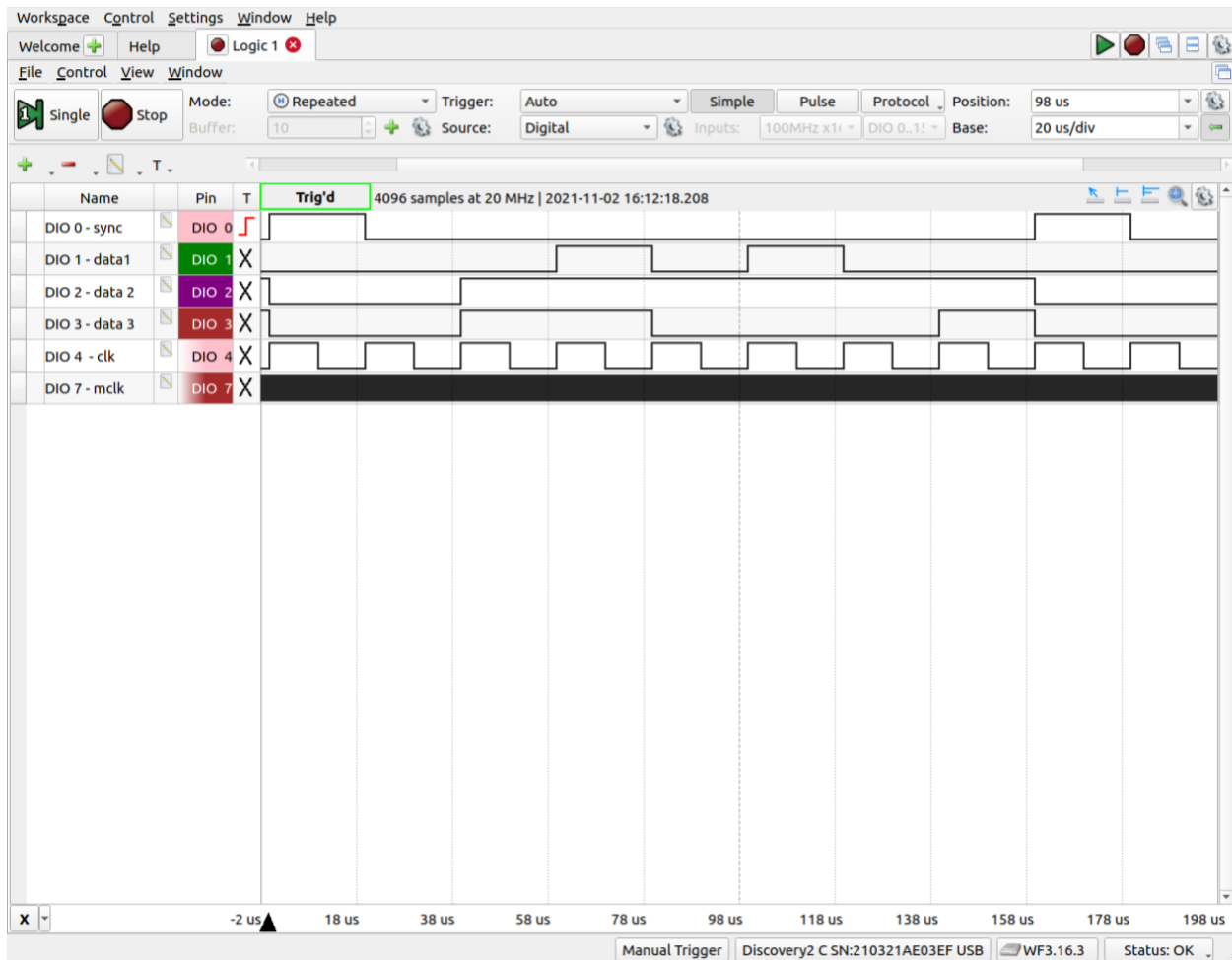


Figure 4: Data recorded on the Analog Discovery

The Code

```

-----
-- Company:
-- Engineer: Eric Walsh & Nicholas Zimmerman
--
-- Create Date: 14:29:41 11/02/2021
-- Design Name:
-- Module Name: Lab6_top_sch - Behavioral
-- Project Name: Digital Design Lab 6
-- Target Devices: Aritix-7 (Xilinx ISE)
-- Tool versions:
-- Description: Generates multiple signals from a 50 MHz clock derived from a 50 GHz master clock
--
-- Dependencies:
--
-- Revision:

```

-- Revision 0.01 - File Created

-- Additional Comments:

--

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;

library UNISIM;

use UNISIM.VComponents.all;

entity Lab6_top_sch is

port(mclk : in std_logic;

sw0 : in std_logic;

Extout : out std_logic_vector(7 downto 0); --using 6 bits out of 8 bits

TEK1 : out std_logic_vector(7 downto 0); --using 6 bits out of 8 bits

TEK5 : out std_logic);

end Lab6_top_sch;

architecture Structural of Lab6_top_sch is

--slow_clock generator

signal clk_next, clk_reg : unsigned(9 downto 0); --2^9=512

signal t_next, t_reg : std_logic;

signal slow_clk : std_logic;

--FSM

signal q,d : unsigned(2 downto 0);

--Generated signals

signal sync, data1, data2, data3 : std_logic;

begin

-- slow_clock generator E.Welch & N. Zimmerman

--

-- Based on L.Aamodt's derived clock generator

process(mclk)

begin

if (mclk'event and mclk='1') then

clk_reg <= clk_next;

t_reg <= t_next; -- T-f/f register

end if;

end process;

clk_next <= (others=>'0') when clk_reg=499 else clk_reg+1;

t_next <= (not t_reg) when clk_reg = 499 else t_reg; --Switch every 500, divide by 1000

```
Clk_Buffer: BUFG  -- Put t_reg on a buffered clock line
port map ( I => t_reg, O => slow_clk);
-- slowclk is a square wave with 50 kHz frequency
```

```
-----
-- Top-level structural architecture      E.Welch & N.Zimmerman
-----
```

```
--DFF
process(slow_clk, sw0)
begin
    if (slow_clk'event and slow_clk='1') then
        q <= d;
    end if;
end process;
--N.S. Logic
d <= (others=>'0') when q=7 else q+1;

--Output Logic (could have used a process with a case statement [type-casting?])
sync <= sw0 and not(q(0)) and not(q(1)) and not(q(2));
data1 <= sw0 and q(0) and (q(2) xor q(1));
data2 <= sw0 and (q(2) or q(1));
data3 <= sw0 and q(1) and (not(q(2)) or q(0));

--Output signals
Extout(0) <= sync;
TEK1(0) <= sync;

Extout(1) <= data1;
TEK1(1) <= data1;

Extout(2) <= data2;
TEK1(2) <= data2;

Extout(3) <= data3;
TEK1(3) <= data3;

Extout(4) <= slow_clk;
TEK1(4) <= slow_clk;

Extout(7) <= mclk;
TEK1(7) <= mclk;
TEK5 <= mclk;

--Unused outputs
```

```
Extout(5) <= '0';  
Extout(6) <= '0';  
TEK1(5) <= '0';  
TEK1(6) <= '0';
```

```
end Structural;
```